

ECE 319H Lab 2

Juan Abusleme - jpa2484

Dr. Mohit Tiwari

Circuit Diagram

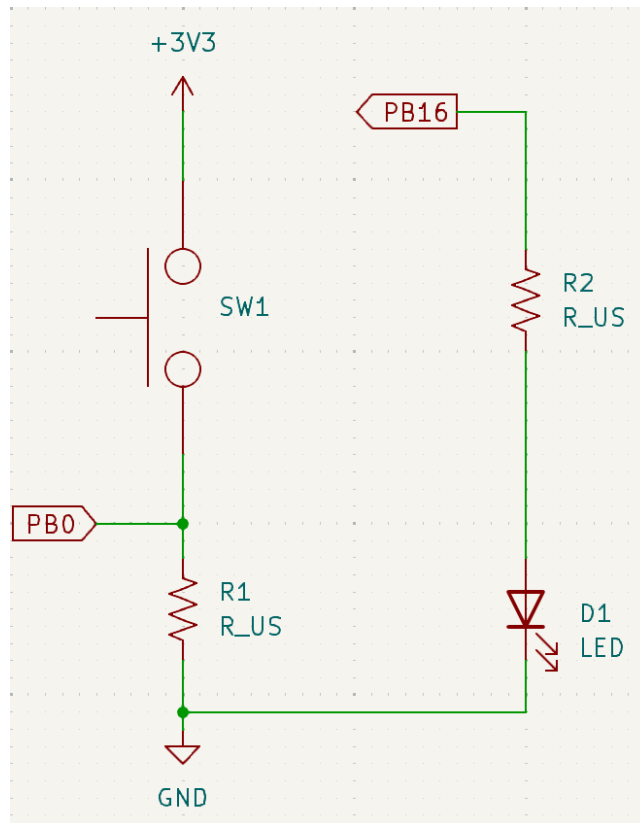


Figure 1: Circuit Diagram of Lab 2 (KiCad)

Estimated LED Voltage and Current

| Parameter | Value | Units | Conditions |
|--------------------|-------|-------|---|
| LED Voltage, V_d | 1.7 | volts | With switch not pressed (Calculated) |
| LED Current, I_d | 2 | mA | With switch not pressed (Calculated) |

Table 1: Estimated Table

Switch measurements

| Parameter | Value | Units | Conditions |
|----------------------|-------|-------|--|
| Input Voltage on PB0 | 0 | volts | With switch not pressed (measured with voltmeter) |
| Resistor current | 0 | mA | With switch not pressed (measured with ammeter) |
| Input Voltage on PB0 | 3.3 | volts | With switch pressed (measured with voltmeter) |
| Resistor current | 0.33 | mA | With switch pressed (measured with ammeter) |

Table 2: Switch measurements

LED Voltage and Current measurements

| Parameter | Value | Units | Conditions |
|-----------------------------|-------|-------|--|
| LED Voltage, V_d | 0 | volts | With LED off (measured with voltmeter) |
| LED Current, I_d | 0 | mA | With LED off (measured with ammeter) |
| LED Voltage, V_d | 1.762 | volts | With LED on (measured with voltmeter) |
| LED Current, I_d | 2.8 | mA | With LED on (measured with ammeter) |
| LED Power, $V_d \times I_d$ | 4.934 | mW | With LED on (multiply two measurements) |

Table 3: LED measurements.

Calculated current: $I_d = 20 \cdot V_d - 32 = 20 \cdot 1.762 - 32 = 3.24$

Logic Analyzer Image

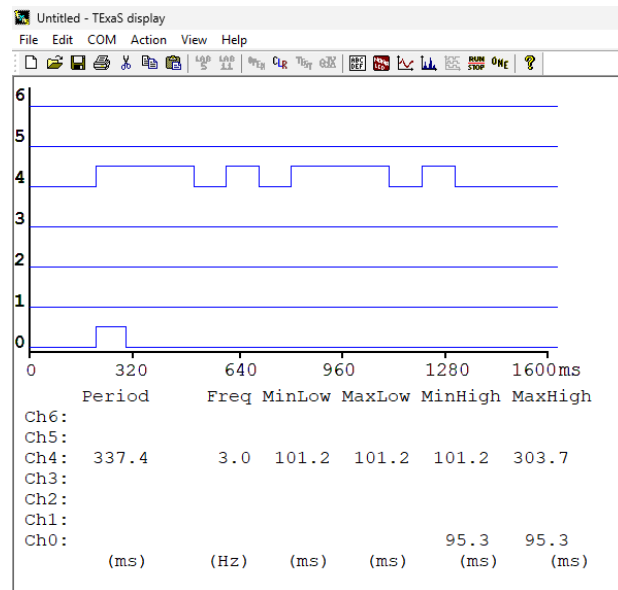


Figure 2: Logic Analyzer showing one letter

Terminal window of autograder

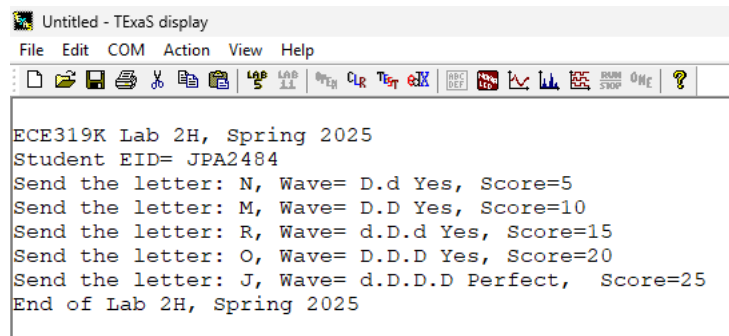


Figure 3: Complete Autograder for Lab 2H